

Hybrid (h) Parameters

By

Dr. Ravinder Nath Rajotiya

Hybrid or h parameter

- Widely used in modeling electronic components and circuits particularly the transistor. It is called hybrid because both the open and short circuit parameters are used.
- Here the difference with the Z and Y parameter is that we use voltage at one port and the current at the other port

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Forming the equations

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

h Parameters

- Forming the equations

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

- Assuming short circuit at output port so $V_2=0$

$$V_1 = h_{11}I_1 \quad \text{or} \quad h_{11} = V_1 / I_1 \quad .$$

$$I_2 = h_{21}I_1 \quad \text{or} \quad h_{21} = I_2 / I_1$$

h_{11} is called as input impedance measured in Ohms while h_{21} is forward current gain which is unitless quantity

- Now assuming the input to be open circuited so $I_1=0$, rewriting the equations we get

$$V_1 = h_{12}V_2 \quad \text{or} \quad h_{12} = V_1 / V_2$$

$$I_2 = h_{22}V_2 \quad \text{or} \quad h_{22} = I_2 / V_2$$


- h_{12} is called as reverse voltage gain and h_{22} is called output admittance of the circuit.
- The equivalent circuit of the h parameter is shown below:

Equivalent Circuit

From the equations

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

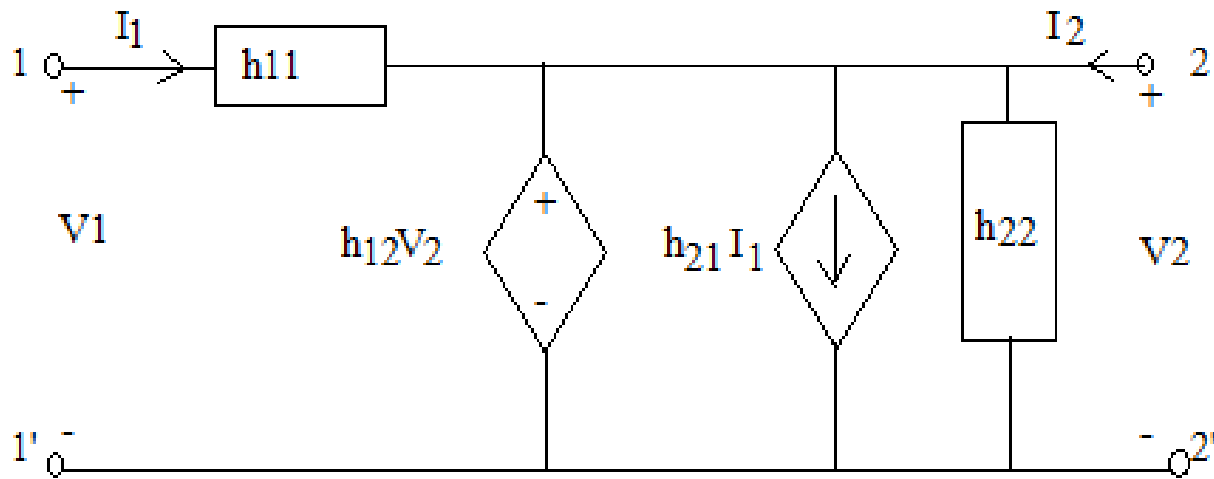

Ex. A common emitter transistor amplifier hardware circuit can be represented by a four terminal network. The signal source strength being 1mV, a resistive load of 10kOhm is applied at the output of the network. The following data is given:

Short circuit input impedance $h_i = 2\text{k}\Omega$

Short circuit forward current ratio $h_f = 50$

Open circuit output admittance $h_o = 25 \times 10^{-6}$.

Open circuit reverse voltage gain $h_r = 3 \times 10^{-4}$.

Express these values in terms of h-parameters, Determine:


- i. h-parameter equivalent circuit
- ii. Voltage drop across the load
- iii. Load current
- iv. Voltage gain
- v. Current Gain

ANS

$$h_{11} = h_i = 2\text{k}\Omega \quad h_{12} = h_r = 3 \times 10^{-4} \quad h_{21} = h_f = 50 \quad h_{22} = h_o = 25 \times 10^{-6}$$

$$\text{H parameter equations being} \quad : \quad V_1 = h_{11}I_1 + h_{12}V_2 \quad I_2 = h_{21}I_1 + h_{22}V_2$$

- (i) Equivalent circuit

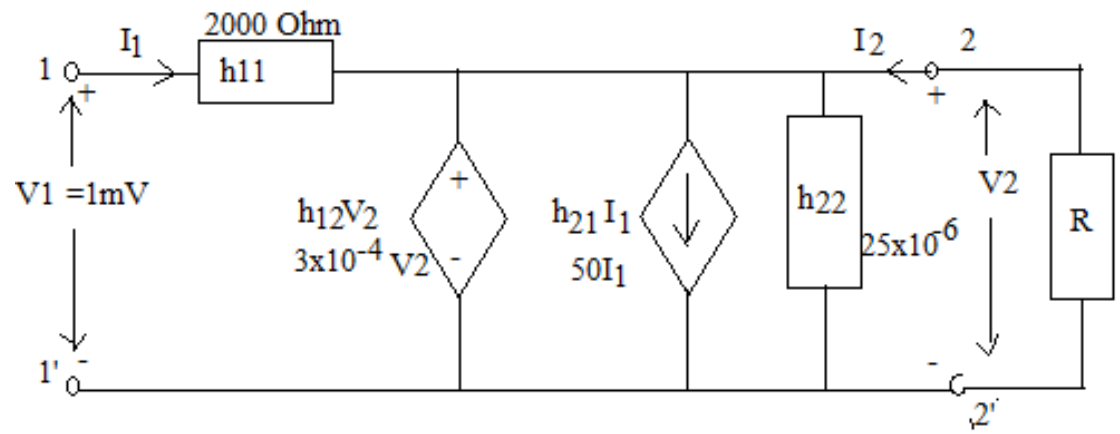

ii. KVL at input port $V_1 = h_{11}I_1 + h_{12}V_2$

$$1\text{mV} = 2000I_1 + 3 \times 10^{-4} V_2$$

$$V_2 = (1 \times 10^{-3} - 2000I_1) / 3 \times 10^{-4} \dots\dots\dots(i)$$

and $I_2 = h_{21}I_1 + h_{22}V_2 = 50I_1 + 3 \times 10^{-4} V_2$

$$-V_2/R = 50I_1 + 25 \times 10^{-6} V_2; -V_2/10 \times 10^3 = 50I_1 + 25 \times 10^{-6} V_2$$

$$-I_1$$

$$-I_1 = (25 \times 10^{-6} + 1/10 \times 10^3) V_2.$$

$$I_1 = (125 \times 10^{-6}) / 50$$

Substituting this value of I_1 in eqn (i) we get:

$$V_2 = (1 \times 10^{-3} - 2000 \times 125 \times 10^{-6} / 50) / 3 \times 10^{-4} = -0.213\text{V}$$


(iii) Load Current

$$I = V_2/R = -0.213 / 10 \times 10^3 = -21.3\mu\text{A} \text{ (-ve means opposite direction)}$$

(iv) Voltage Gain of the circuit $V_2/V_1 = -0.213/0.001 = -213$

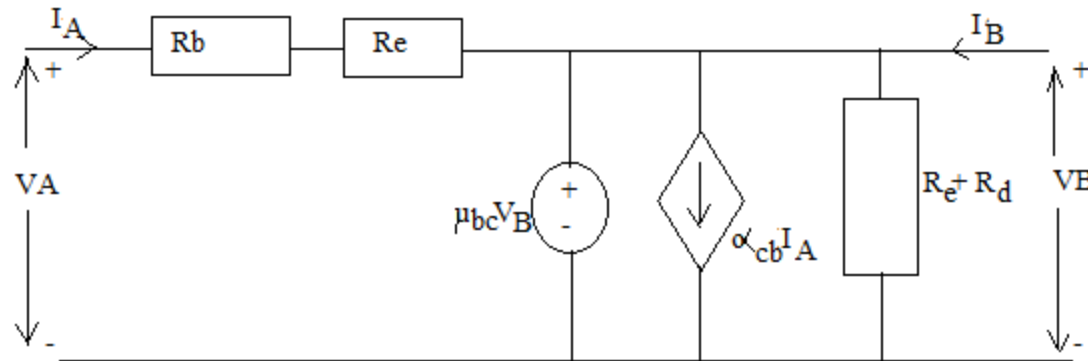(v) Current Gain = I_2/I_1 .

Q. Find the h parameter for the CE transistor equivalent circuit shown below



ANS:

Apply KVL at the input: $V_A = (R_b + R_e)I_A + u_{bc}V_B$

Apply KCL at the output port we get

$$I_B = \alpha_{cb}I_A + V_B/(R_e + R_d)$$

Rearranging in matrix form

Therefore:

$$\begin{bmatrix} V_A \\ I_B \end{bmatrix} = \begin{bmatrix} (R_b + R_e) & u_{bc} \\ \alpha_{cb} & \frac{1}{R_e + R_d} \end{bmatrix} \begin{bmatrix} I_A \\ V_B \end{bmatrix}$$


$$h_{11} = (R_b + R_e);$$

$$h_{12} = u_{bc}$$

$$h_{21} = \alpha_{cb}$$

$$h_{22} = 1/(R_e + R_d)$$

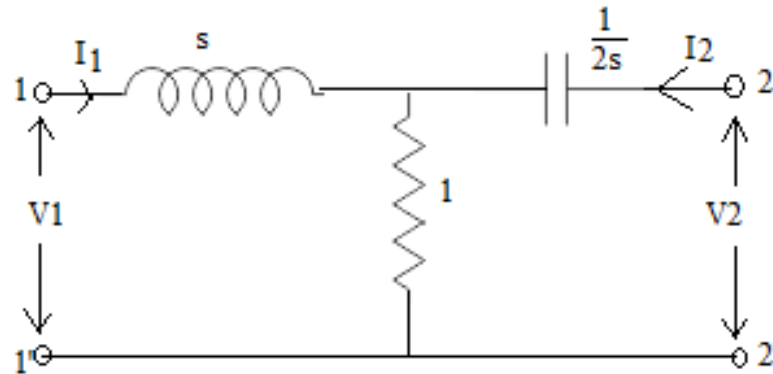HW-1 : For the circuit given below, find the h parameters



HW-2: Determine the h parameters for a transistor in middle frequency range is represented as shown in figure below.

