

Network Analysis and Synthesis



Unit-III

By

Dr. Ravinder Nath Rajotiya

Introduction

- A network is an interconnection of basic electrical elements. A network is called an electric circuit when it has current and voltage sources connected to it. Thus an electric is a closed energized network. Figure below shows an electric network and an electrical circuit.
- A Terminal is an entry or exit point for a current, and a port is a two terminal contacts where current or potential sources are connected or measured. Terminals are used in pairs.

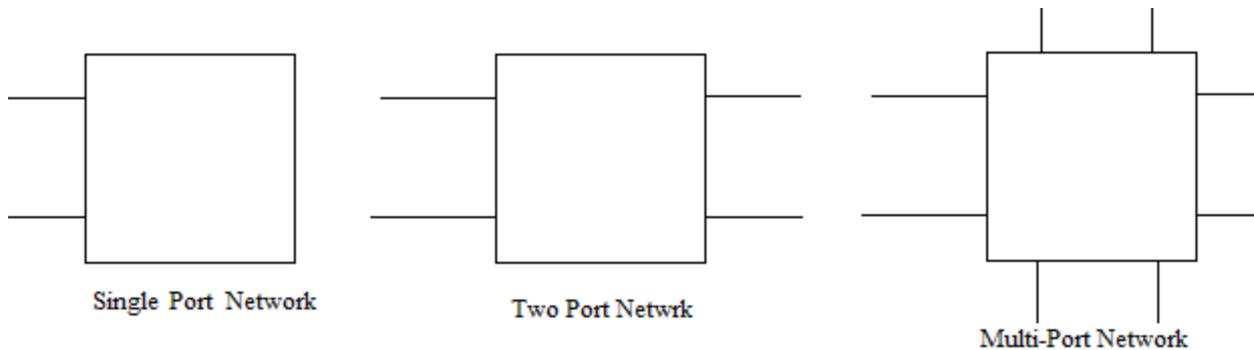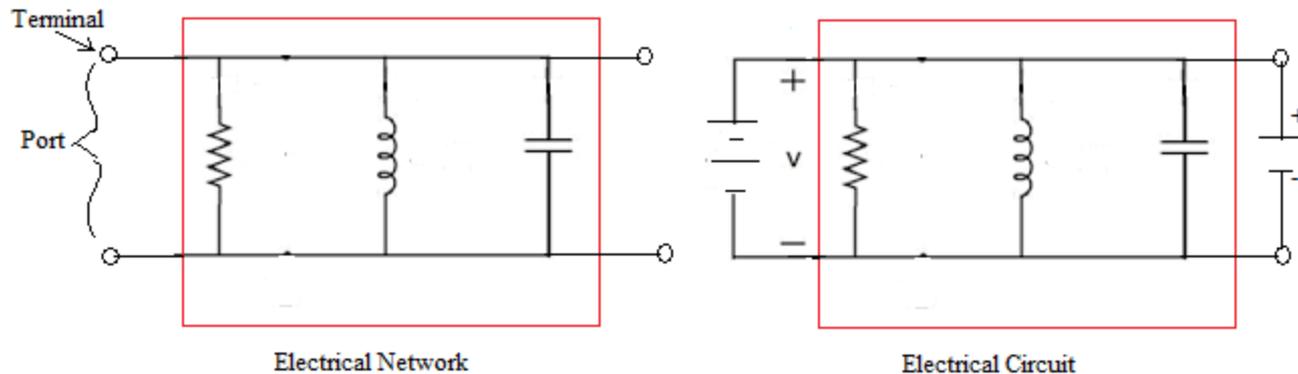


Classification of Electrical Networks


- Based on Terminals: One Port, Two-port or n-port network
- Unilateral or Bilateral
- Linear or Non-Linear
- Active or Passive
- Lumped or Distributed
- Symmetrical or Asymmetrical Network
- Balanced or Unbalanced

Classification based on Configuration

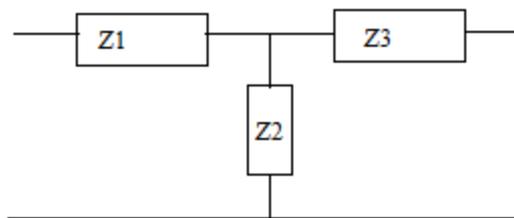
- T Type Network:
 - Symmetrical or Asymmetrical T Networks
 - Balanced or Unbalanced T Networks
 - Half T Section
 - L Section




Asymmetrical T network

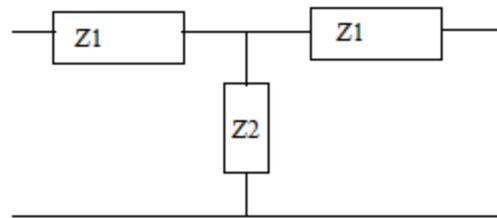


Symmetrical T Network

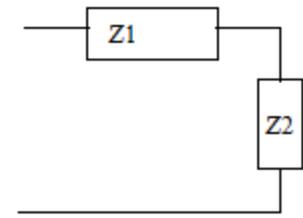

L Section of a T Network

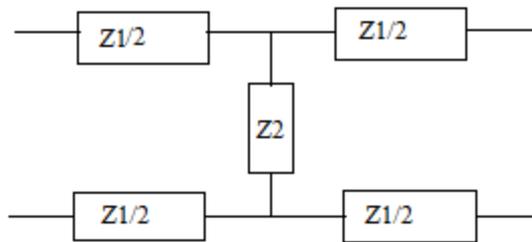


Balanced T Network

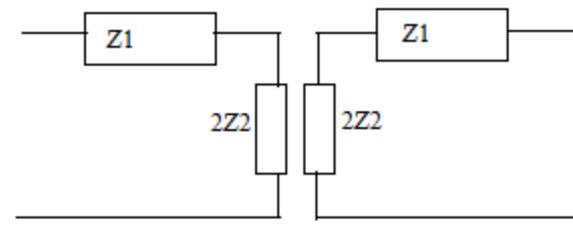


Half Section T Network

Π Network:

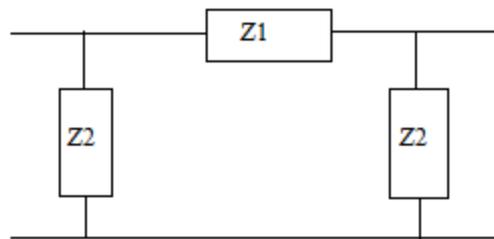
- Symmetrical or Asymmetrical Π networks
- Balanced or Unbalanced Π networks
- Half T Section




Symmetrical Π Network

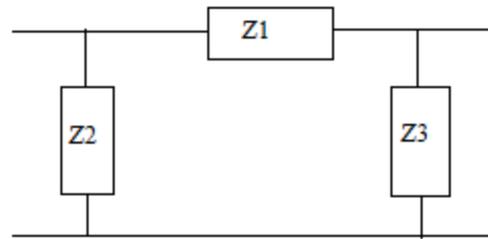

Asymmetrical Π Network

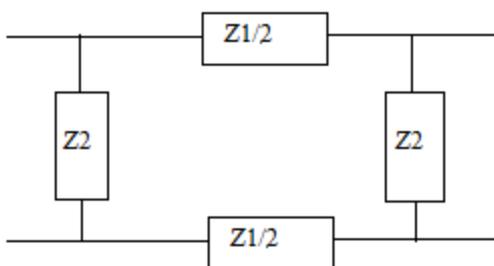


Balanced Π Network

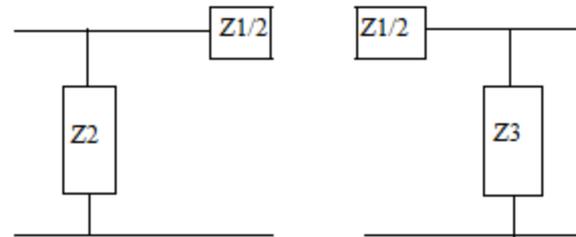


Half Section Asymmetrical Π Network


Lattice and Bridged Networks

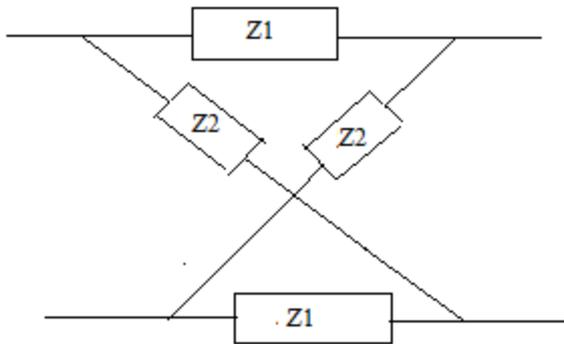

Symmetrical Lattice Network

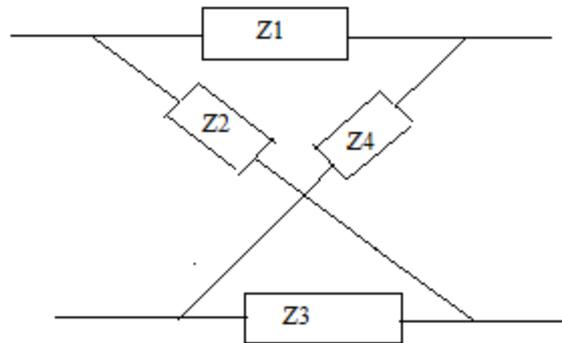

Asymmetrical Lattice Network

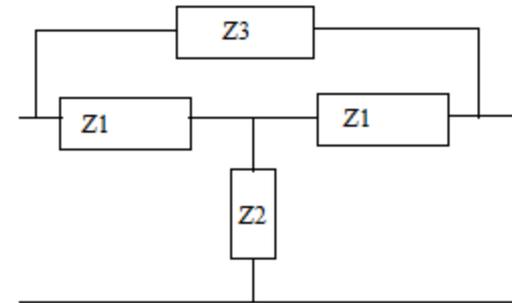

Bridged T Network

Network parameters (Based on I/O Voltage and Current)


Z, Y, h, ABCD pPARAMETERS

- Z Parameter (Open Circuit Impedance) $Z_{11}, Z_{12}, Z_{21}, Z_{22}$
 - This parameter is determined by first opening the output terminal and writing the KVL equations, then opening the input terminal and writing the KVL equation for V_2 . We can then solve the equations by any method like Cramer's rule to determine the Y parameters.
- Y parameter (Short Circuit Admittance) $Y_{11}, Y_{12}, Y_{21}, Y_{22}$,
 - This parameter is found by first shorting the output terminal and then writing the KVL equation for I_1 and then shorting the input terminal and writing the KVL equation for I_2 . We can then solve the equations by any method like Cramer's rule to determine the Y parameters.
- Hybrid (h) Parameter $h_{11}, h_{12}, h_{21}, h_{22}$,
 - The h parameter make use of the hybrid approach that is it uses both the open circuit and short circuit approach. First we short the output terminal and write the equation for V_1 , then we open the input terminal and write the equation for I_2 . We can then solve the equations by any method like Cramer's rule to determine the h parameters.
- Inverse hybrid (g) Parameter $g_{11}, g_{12}, g_{21}, g_{22}$,
 - This is the dual of the h parameter representation and the equation is written as
(I_1, V_2) = f(V_1, I_2) where V_1 and I_2 are independent variables.

Transmission Parameters

- ABCD (Transmission) Parameter A, B, C, D
 - Transmission parameters are used in the analysis of power transmission lines, where they are also known as 'general circuit parameters. They are also known as Chain parameters or ABCD parameters. The general equations are written as: $(V_1, I_1) = f(V_2, I_2)$
- Inverse Transmission Parameter A', B', C', D'
 - This is the dual of the transmission parameters. The equation for this parameter is written as : $(V_2, I_2) = f(V_1, I_1)$

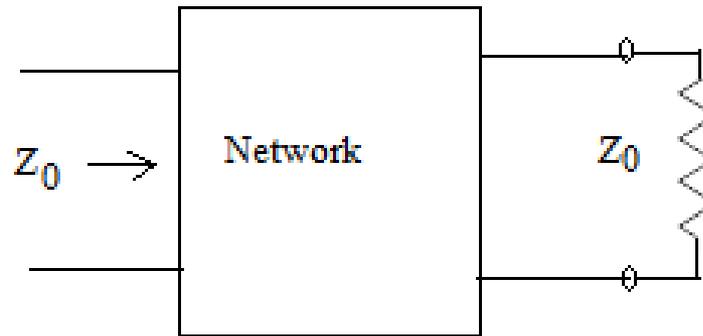- Characteristics of Symmetrical Networks
 - Characteristic Impedance (Z_0): It is the impedance measured at the input port of a network when the infinite no. of network elements are connected



- Propagation Constant: It is defined as the ration of the current or voltage entering the network to the current or voltage leaving the network

Characteristics of Asymmetrical Networks

Iterative Impedance: It is the input impedance of a network with infinite sections at one port or the impedance measured at one port when other port is shunted with its input impedance with infinite network sections.


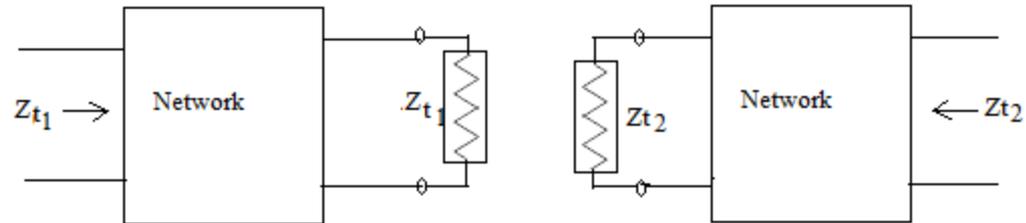


Image Impedance: Let Z_{i1} and Z_{i2} be two impedances such that Z_{i1} is the driving point impedance at port-1 with impedance Z_{i2} connected across Port-2 and Z_{i2} is the driving point impedance at port-2 with Z_{i1} connected across port-1, then the impedances Z_{i1} and Z_{i2} are called image impedance of the network.

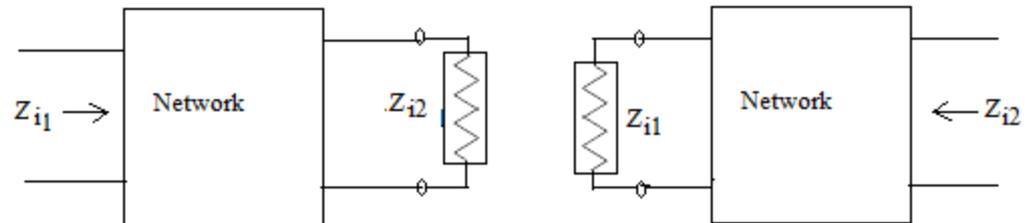

Iterative transfer Constant: If an asymmetrical network is terminated with iterative impedance, then the factors affecting the energy propagation are defined in terms of iterative transfer constant Q_t . It is a complex number.

Image Transfer Constant: In asymmetrical networks, the factors affecting the propagation of energy is defined in terms of image transfer constant Q_i if the network is terminated in image impedance.