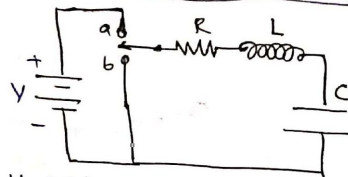


Time Domain Solution of RLC Circuit

When the s/w is at 'a' the circuit has gained steady state



$\therefore V_C(0^-) = V = V_C(0^+)$ and then capacitor acts as open so

$$i(0^-) = 0 = i(0^+)$$

When s/w is moved to position 'b'

Applying KVL

$$R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 0 \quad \text{--- (1)}$$

differentiating

$$R \cdot \frac{d}{dt} i(t) + L \cdot \frac{d^2}{dt^2} i(t) + \frac{1}{C} i(t) = 0$$

$$\text{or } \frac{d^2}{dt^2} i + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

The characteristic eqn.

$$(D^2 + \frac{R}{L} D + \frac{1}{LC}) i = 0$$

$$\text{or } D^2 + \frac{R}{L} D + \frac{1}{LC} = 0$$

$$D_1, D_2 = \frac{-R/L \pm \sqrt{(R/L)^2 - 4/LC}}{2}$$

Therefore

$$i(t) = K_1 e^{D_1 t} + K_2 e^{D_2 t} \quad \text{--- (1)}$$

K_1 and K_2 are arbitrary constants determined by initial conditions

$$i(0^-) = i(0^+) = 0, \quad v_C(0^-) = v_C(0^+) = 0$$

Put these in eqn. (1)

$$R i(0) + \frac{1}{L} \frac{di(0)}{dt} + \frac{1}{C} \int i(t) \Big|_{t=0} = 0$$

$$0 + \frac{1}{L} \frac{di(0^+)}{dt} + V = 0$$

$$\therefore \frac{di(0^+)}{dt} = -VL \text{ Amp/sec}$$

Applying initial condition in (1) at $t=0$

$$0 = K_1 + K_2 \quad \text{--- (1*)}$$

differentiating eqn. (1)

$$\frac{di}{dt} = K_1 D_1 e^{D_1 t} + K_2 D_2 e^{D_2 t}$$

$$\text{at } t=0 \quad \frac{di}{dt} = -VL$$


Substituting

$$-VL = K_1 D_1 + K_2 D_2 \quad \text{--- (IV)}$$

from (1*) and (IV) the value of K_1 and K_2 can be determined and substituted in (1).

— x —

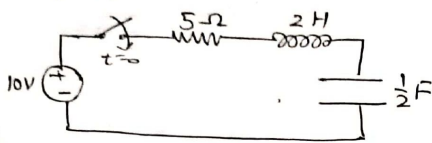Q. Find the expression for current $i(t)$ for $t > 0$ if s/w is closed at time $t = 0$



Applying KVL

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 10$$

$$5i + 2 \frac{di}{dt} + 2 \int i dt = 10$$

differentiating we get

$$\frac{d^2 i}{dt^2} + 2.5 \frac{di}{dt} + 2i = 0 \quad \text{--- (1)}$$

write the characteristic Eqn.

$$D^2 + 2.5D + 1 = 0$$

Roots of this eqn.

$$D_1, D_2 = \frac{-2.5 \pm \sqrt{(2.5)^2 - 4}}{2}$$

$$= -0.5, -2$$

∴ The current eqn.

$$i(t) = K_1 e^{-0.5t} + K_2 e^{-2t} \quad \text{--- (11)}$$

Initial condition

Assume, Before the s/w is closed, the circuit was deenergized

$$\therefore i(0^-) = i(0^+) = 0 \quad V_C(0^-) = V_C(0^+) = 0$$

Applying initial condition to eqn. (1) at $t = 0$

$$5 \times 0 + 2 \cdot \frac{di}{dt} + 2 \times 0 = 10 \quad ; \quad \frac{di}{dt} = 5$$

$$0 = K_1 + K_2 \quad \text{--- (11)}$$

differentiating eqn. (ii)

$$\frac{di}{dt} = -0.5 K_1 e^{-0.5t} - 2 K_2 e^{-2t}$$

at $t = 0$ Applying initial condition at $t = 0$

$$5 = -0.5 K_1 + 2 K_2 \quad \text{--- (1V)}$$

from (11) and (1V) (multiplying 11) by 0.5

$$0.5 \times \text{eqn. (11)} \quad \begin{aligned} 0.5 K_1 + 0.5 K_2 &= 0 \\ -0.5 K_1 - 2 K_2 &= 5 \end{aligned}$$

$$-1.5 K_2 = 5$$

$$K_2 = \frac{-5}{1.5} = -3.33$$

Putting value of K_2 in eqn. (11)

$$K_1 - \frac{5}{1.5} = 0$$

$$K_1 = \frac{5}{1.5} = 3.33$$

Putting K_1, K_2 in eqn. (11)

$$i(t) = 3.33 \left[e^{-0.5t} - e^{-2t} \right]$$