

# Open and Short Circuit Parameters

By

Dr. Ravinder Nath Rajotiya

# Finding the Open Circuit Parameters or Z Parameters $Z_{11}, Z_{12}, Z_{21}, Z_{22}$

- We can find the network parameters by solving the network equations written using the loop or the nodal methods
- The Loop equations can be written as :

$$V_1 = I_1 Z_{11} + I_2 Z_{12} + I_3 Z_{13} \dots \dots \dots I_n Z_{1n}$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22} + I_3 Z_{23} \dots \dots \dots I_n Z_{2n}$$

$$V_3 = I_1 Z_{31} + I_2 Z_{32} + I_3 Z_{33} \dots \dots \dots I_n Z_{3n}$$

-

-

$$V_n = I_1 Z_{n1} + I_2 Z_{n2} + I_3 Z_{n3} \dots \dots \dots I_n Z_{nn}$$

# Loop Equation

$$V_1 = I_1 Z_{11} + I_2 Z_{12} + I_3 Z_{13} \dots I_n Z_{1n}$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22} + I_3 Z_{23} \dots I_n Z_{2n}$$

$$V_3 = I_1 Z_{31} + I_2 Z_{32} + I_3 Z_{33} \dots I_n Z_{3n}$$

-  
-

$$V_n = I_1 Z_{n1} + I_2 Z_{n2} + I_3 Z_{n3} \dots I_n Z_{nn}$$

In Matrix Form

$$[V] = [Z] [I]$$

$$\text{or } V = \Delta Z \times I$$

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ - \\ - \\ V_n \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \dots & Z_{1n} \\ Z_{21} & Z_{22} & Z_{23} \dots & Z_{2n} \\ Z_{31} & Z_{32} & Z_{33} \dots & Z_{3n} \\ - & - & - & - \\ - & - & - & - \\ Z_{n1} & Z_{n2} & Z_{n3} \dots & Z_{nn} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ - \\ - \\ I_n \end{bmatrix}$$

# Finding Z

$$\Delta Z = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \dots & Z_{1n} \\ Z_{21} & Z_{22} & Z_{23} \dots & Z_{2n} \\ Z_{31} & Z_{32} & Z_{33} \dots & Z_{3n} \\ \dots & \dots & \dots & \dots \\ Z_{n1} & Z_{n2} & Z_{n3} \dots & Z_{nn} \end{bmatrix}$$

$$\Delta Z_{11} = \begin{bmatrix} Z_{22} & Z_{23} \dots & Z_{2n} \\ Z_{32} & Z_{33} \dots & Z_{3n} \\ \dots & \dots & \dots \\ Z_{n2} & Z_{n3} \dots & Z_{nn} \end{bmatrix}$$

Then we can find the input impedance as:  $Z_{in} = \Delta Z / \Delta Z_{11}$ . We can similarly write all Z parameters like  $Z_{12}$ ,  $Z_{21}$ , ... Using Cramer's Rule

# Two Port Network

- We can write the equations for the dependent variable in terms of the independent variables

$$(V_1, V_2) = f(I_1, I_2)$$

$$[V] = [Z][I]$$

- For a two-port network

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

# Z Parameter

- In order to determine the open circuit impedance or the Z parameter, open the input port and apply the excitation at the output port. Since the input is open  $I_1=0$ , we then determine the  $I_2$  and  $V_1$  to obtain  $Z_{12}$  and  $Z_{22}$ .
- When  $I_1 = 0$ , the equation reduces to
  - $V_1 = Z_{12} I_2$  ; so we get  $Z_{12} = V_1 / I_2$
  - $V_2 = Z_{22} I_2$  ; so we get  $Z_{22} = V_2 / I_2$
- Then open the output port so that  $I_2=0$ , and determine the  $I_1$  and  $V_2$  to obtain  $Z_{11}$  and  $Z_{21}$  . When  $I_2 = 0$ , the equation reduces to
  - $V_1 = Z_{11} I_1$  ; so we get  $Z_{11} = V_1 / I_1$
  - $V_2 = Z_{21} I_1$  ; so we get  $Z_{21} = V_2 / I_1$

# Equivalent Circuit of Loop equations

- We know the two loop equations:


$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$


- Rewriting these equations remembering that  $Z_{12}I_2$  and  $Z_{21}I_1$  are current controlled voltage sources (CCVS)

$$V_1 = (Z_{11} - Z_{12})I_1 + Z_{12}(I_1 + I_2)$$
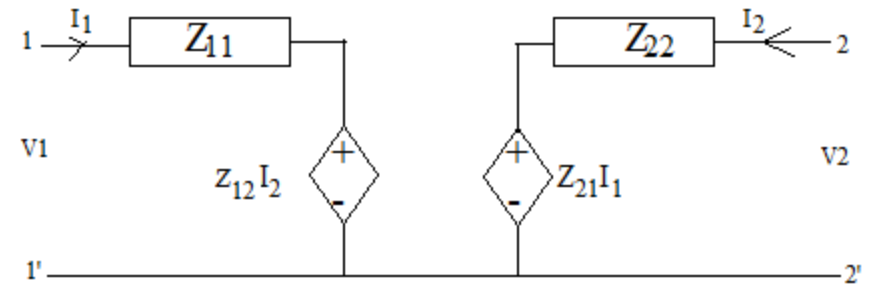
$$V_2 = (Z_{21} - Z_{12})I_1 + (Z_{22} - Z_{12})I_2 + Z_{12}(I_1 + I_2)$$



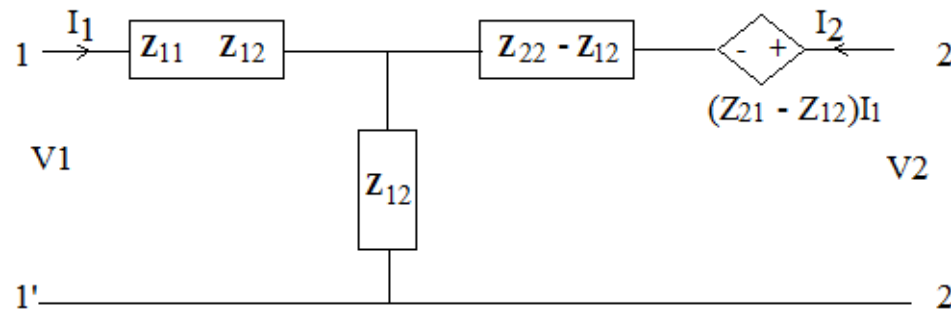(a) Equivalent Circuit of  $V_1 = (Z_{11} - Z_{12})I_1 + Z_{12}(I_1 + I_2)$



(b) Equivalent circuit of  $V_2 = (Z_{21} - Z_{12})I_1 + (Z_{22} - Z_{12})I_2 + Z_{12}(I_1 + I_2)$

# Short Circuit Admittance (Y)

- The short circuit admittance is found by writing the node equations. These equations help us to write the dependent variables in terms of the independent variable as:

- $(I_1, I_2) = f(V_1, V_2)$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Which can be written in matrix form as:

$$[I] = [Y][V]$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



# Admittance Parameters

- First we short the output terminal, so  $V_2=0$   
substituting we get:

$$I_1 = Y_{11} V_1 \quad \text{or} \quad Y_{11} = I_1 / V_1$$

$$I_2 = Y_{21} V_1 \quad \text{or} \quad Y_{21} = I_2 / V_1$$

- Then we short circuit the input port , so  $V_1=0$

$$I_1 = Y_{12} V_2 \quad \text{or} \quad Y_{12} = I_1 / V_2$$


$$I_2 = Y_{22} V_2 \quad \text{or} \quad Y_{22} = I_2 / V_2$$

# Equivalent Circuit in terms of admittance


The equivalent circuit equations can be written by rearranging the above equation:

$$I_1 = (Y_{11} + Y_{12})V_1 + Y_{12}(V_1 - V_2)$$
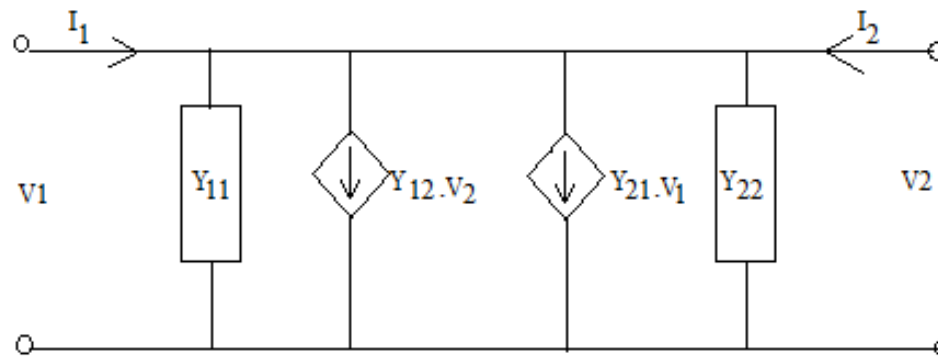
$$I_2 = (Y_{21} - Y_{12})V_1 + (Y_{22} - Y_{12})V_2 + Y_{12}(V_2 - V_1)$$



(a) Y Parameter Equivalent Circuit

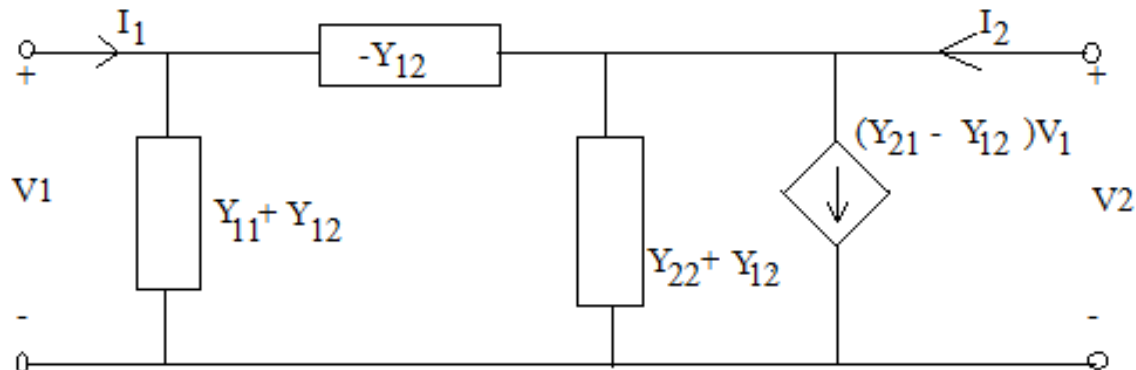

# Star-Delta Transformation

- The use of star-delta and delta-star sometimes helps in simplifying the network.
- **Delta-Star Transformation:**

Given  $Z_1, Z_2, Z_3$  then

1. Delta star Transformation

- Let  $Z_1, Z_2, Z_3$  be impedance in delta then
- 

$$Z_a = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z_b = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z_c = \frac{Z_3 Z_1}{Z_1 + Z_2 + Z_3}$$

## •Star-Delta Transformation


- Let  $Z_a, Z_b, Z_c$  be the impedances in star network then the impedance of delta network will be:

$$Z_1 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$


$$Z_2 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$

$$Z_3 = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$

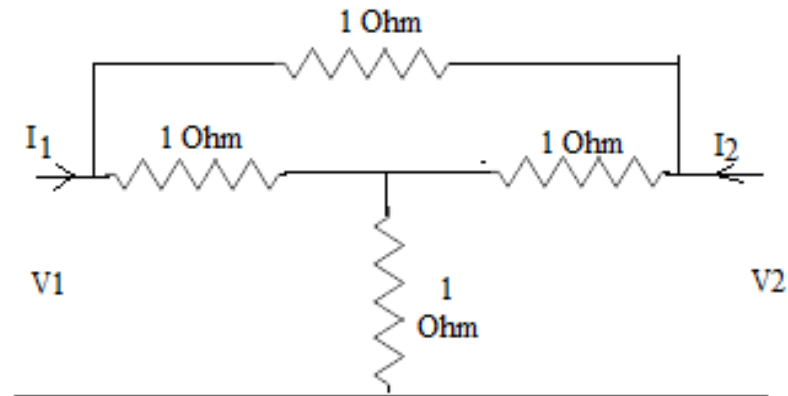Ex. Determine the Y parameter of the following network



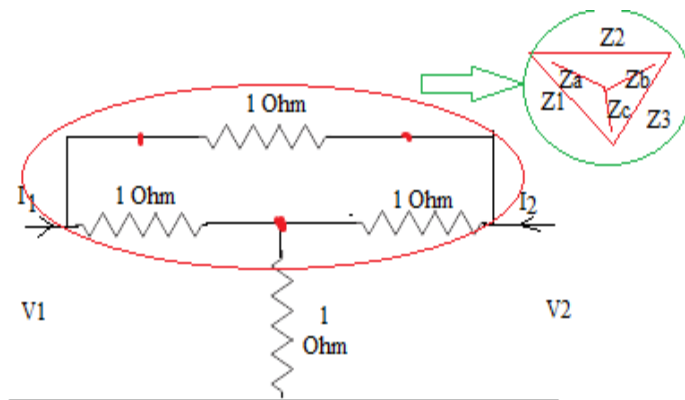- Ans:
- We know the Y-parameter equations :
- $I_1 = Y_{11}V_1 + Y_{12}V_2$
- $I_2 = Y_{21}V_1 + Y_{22}V_2$
- Let us first transform the delta connection at the top to star




$$Z_a = \frac{1 \times 1}{1 + 1 + 1} = \frac{1}{3}$$

$$Z_b = \frac{1 \times 1}{1 + 1 + 1} = \frac{1}{3}$$

$$Z_c = \frac{1 \times 1}{1 + 1 + 1} = \frac{1}{3}$$

# So, the simplified network becomes:

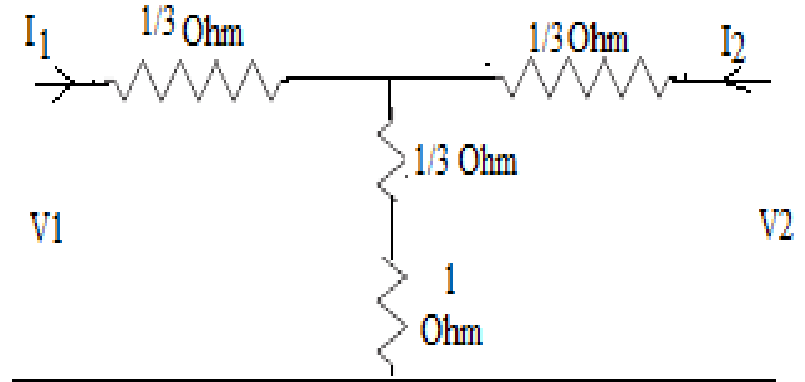

Shorting the output port,  $V_2=0$

Therefore

$$V_1 - \frac{1}{3}I_1 - \frac{4}{3}(I_1 + I_2) = 0 \quad \rightarrow \quad V_1 - \frac{5}{3}I_1 - \frac{4}{3}I_2 = 0 \quad (1)$$

$$\text{and} \quad -\frac{1}{3}I_2 - \frac{4}{3}(I_2 - I_1) = 0 \quad \rightarrow \quad -\frac{5}{3}I_2 - \frac{4}{3}I_1 = 0$$

$$\text{solving we get } I_2 = -\frac{4}{5}I_1 \quad \text{and } I_1 = -\frac{5}{4}I_2. \quad (2)$$

Substituting  $I_2$  from eqn (2) in eqn (1) we get

$$V_1 - \frac{5}{3}I_1 - \frac{4}{3}\left(-\frac{4}{5}I_1\right) = 0$$

$$\text{Or } V_1 = \frac{9}{15}I_1 \quad (3)$$

$$\text{Therefore } Y_{11} = I_1/V_1 = 15/9$$

$$Y_{11} = \mathbf{5/3 \text{ mho}} \quad (4)$$

$$\text{and also } V_1 = \frac{9}{15} \times \left(-\frac{5}{4}I_2\right)$$


$$\text{So } V_1 = \frac{3}{4}I_2 \quad (\text{Ignoring direction})$$

$$Y_{21} = I_2 / V_1 = \mathbf{4/3 \text{ mho}} \quad (5)$$

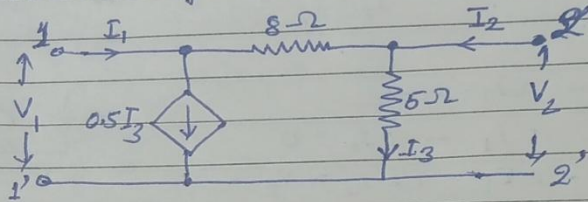- **(ii) Now short circuiting at the input port,  $V_1=0$**
- Applying KVL again
- $V_2 - 1/3I_2 - 4/3(I_2 + I_1) = 0 \quad \rightarrow V_2 - 5/3I_2 - 4/3 I_1 = 0 \quad \text{---(6)}$
- and  $- 1/3 I_1 - 4/3 (I_1 + I_2) = 0 \quad \rightarrow - 5/3I_1 - 4/3I_2 = 0 \quad \text{or}$
- $I_1 = -4/5 I_2 \quad \text{and } I_2 = -5/4I_1$   
(7)
- Substituting  $I_1$  in eqn (6) we get
- $V_2 - 5/3I_2 - 4/3 (-4/5I_2) = 0 \quad V_2 = 9/15I_2$   
(8)
- so,  $Y_{22} = I_2/V_2 = 15/9$
- Or  $Y_{22} = 5/3 \text{ mho}$
- From (7) and (8)  $V_2 = 9/15 \times (5/4I_1) = 3/4I_1$
- So  $V_2 = 3/4I_1$
- $Y_{12} = I_1/V_2 = 4/3 \text{ mho}$

Que

A  $\Pi$  network has been shown in figure below, where  $0.5I_3$  is the controlled current source. Obtain the  $Z$ -parameters for this circuit



Sol.  $\Rightarrow$  With off open circuit at port 2-2'

Potential at node c-d = V.

$$I_1 = I_3 + 0.5I_3$$

$$= 1.5I_3$$

But  $I_3 = \frac{V_{c-d}}{R} = \frac{V_1}{8+5} = \frac{V_1}{13}$

$$\therefore I_1 = \frac{1.5 \times V_1}{13} \text{ Amp}$$

Also  $V_{c-d} = V_2 = I_3 \times 5 = \frac{V_1}{13} \times 5 = \frac{5V_1}{13}$

$$\therefore V_2 = \frac{5V_1}{13}$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{5V_1 \times 13}{13 \times 1.5V_1} = 3.33\Omega$$

Therefore  $Z_{11} = \frac{V_1}{I_1} = \frac{V_1}{1.5 \frac{V_1}{13}}$  OR

$$Z_{11} = \frac{13}{1.5} = 8.67\Omega$$

$\Rightarrow$  Now open the input port so that  $I_1 = 0$

As seen

$$I_2 = I_3 + 0.5I_3 =$$

$$I_2 = 1.5I_3$$

Loop-1  $5I_3 - 8 \times 0.5I_3 = V_{c-d}$

$$\therefore V_1 = 5I_3 - 4I_3$$

$$V_1 = I_3$$


but  $V_{c-d} \equiv V_1$   
and  $5I_3 \equiv V_2$

$$\therefore Z_{22} = \frac{V_2}{I_2} = \frac{5I_3}{1.5I_3}$$

$$Z_{22} = 3.33\Omega$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{I_3}{1.5I_3}$$

$$Z_{12} = 0.67\Omega$$

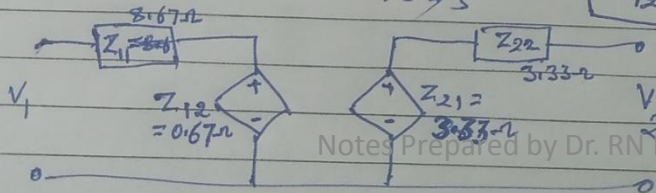


# Questions

1. For the following network:

(a) Find the open circuit impedance and draw the equivalent circuit

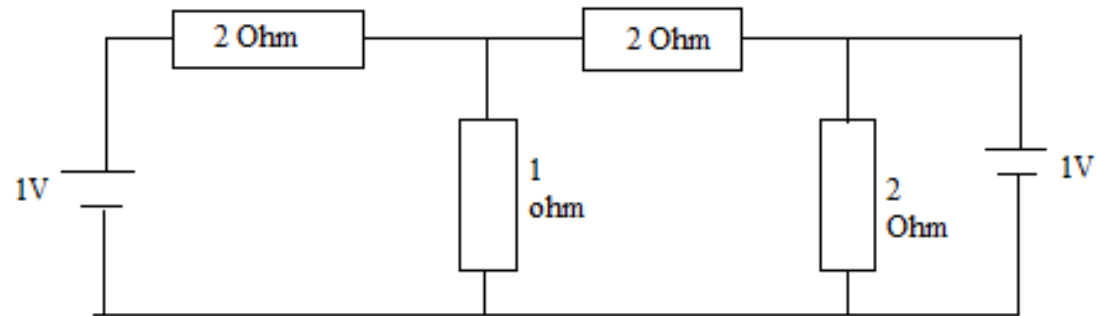(b) Find the short circuit admittance and draw the equivalent circuit



2. For the following network, Determine the Z parameter

