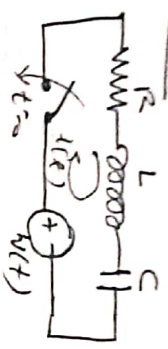


## S-Domain Series-RLC Circuit

Assuming L, C are initially uncharged and s/w closed at  $t=0$



$\therefore$  at  $t=0$ :  $i(0^-) = i(0^+) = 0$   
and  $v_C(0^-) = v_C(0^+) = 0$

Applying KVL at  $t > 0$

$$R \cdot i(t) + L \cdot \frac{di}{dt} + \frac{1}{C} \int i dt = v(t)$$

Applying Laplace Transformation

$$R I(s) + s L I(s) - L i(0) + \frac{I(s)}{C s} + v_C(0) = V(s)$$

$$I(s) [R + sL + \frac{1}{Cs}] = V(s)$$

$$I(s) = \frac{\frac{1}{Cs} V(s)}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{s \cdot V(s)}{L(s^2 + \frac{R}{L}s + \frac{1}{LC})}$$

where  $s_1, s_2 = -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - \frac{1}{LC}}$

$$I(s) = \frac{V}{L} \cdot \frac{1}{(s-s_1)(s-s_2)}$$

solving =  $\frac{V}{L} \cdot \frac{1}{(s-s_1)(s-s_2)} = \frac{A}{s-s_1} + \frac{B}{s-s_2}$

$$A = \frac{V}{L} \cdot \frac{1}{(s_1-s_2)}$$

$$B = \frac{V}{L} \cdot \frac{1}{(s_2-s_1)}$$

cont...

So, we get

$$I(s) = \frac{V}{L(s_1-s_2)} \left[ \frac{1}{s-s_1} - \frac{1}{s-s_2} \right]$$

$$i(t) = \frac{V}{L(s_1-s_2)} \left[ e^{s_1 t} - e^{s_2 t} \right]$$

$s_1 = s_2$  Roots are same

$$I(s) = \frac{V/L}{(s-s_1)^2}$$

Taking inverse  $i(t) = \frac{V}{L} t \cdot e^{s_1 t}$

### DAMPING

OVER DAMPED  $\frac{1}{4}$

Roots are distinct

(1) overdamped  $(\frac{R}{2L})^2 > \frac{1}{LC}$

Critically Damped  
If roots are  $-r$ , Real, Repeated

$$(\frac{R}{2L})^2 = \frac{1}{LC}$$


Under Damped  
Complex conjugate roots

$$(\frac{R}{2L})^2 < \frac{1}{LC}$$

Q. Find  $i(t)$  in the circuit shown in figure, if s/w is closed at  $t=0$

Sol.

Taking Laplace of circuit and Redrawing

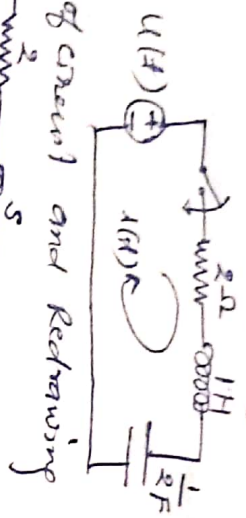

$$I(s) \left[ 2 + s + \frac{2}{s} \right] = \frac{1}{s}$$

$$I(s) \left[ \frac{s^2 + 2s + 2}{s} \right] = \frac{1}{s}$$


$$I(s) = \frac{1}{s} \times \frac{s}{s^2 + 2s + 2}$$

$$= \frac{1}{(s+1)^2 + (1)^2}$$

Taking Inverse Laplace we get


$$i(t) = e^{-t} \cdot \sin(t)$$

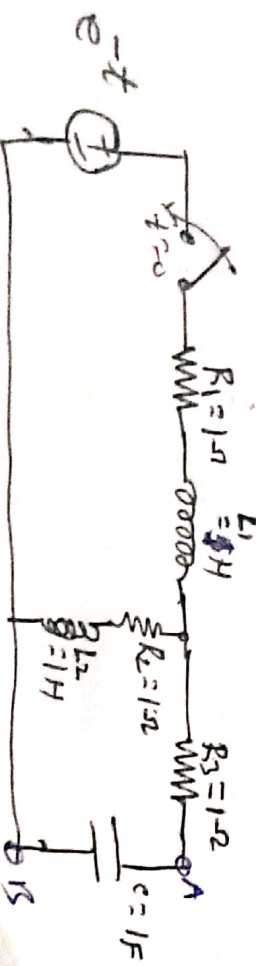Q. In a related circuit, the s/w is closed at time  $t=0$ . Drawing Laplace transform network, and using Thevenin theorem find  $i(t)$  in resistor  $R_3$




Sol.

(1) Drawing Laplace of the circuit

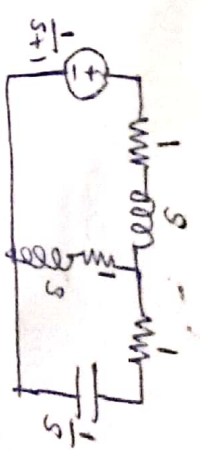

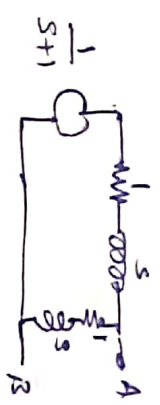(2) Applying Thevenin theorem, (Remove load and short voltage sources)



Two impedance are in parallel

$$Z_{AB} = \frac{1+s}{1+s} \parallel \frac{1}{s} = \frac{(1+s)(1+s)}{1+s+1+s} = \frac{(1+s)^2}{2(s+1)}$$


$$Z_{AB} = \frac{s+1}{2}$$

$$\text{By voltage division } V_{AB} = V_{TH} = V \times \frac{Z_{AB}}{Z_T}$$

$$= \frac{1}{s+1} \times \frac{s+1}{2(s+1)}$$

$$V_{TH} = \frac{1}{2(s+1)}$$

Therefore the Thevenin equivalent is:

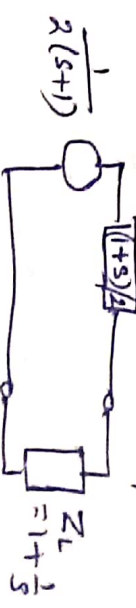

$$I(s) = \frac{\frac{1}{2(s+1)}}{2 + 1 + \frac{1}{s}} = \frac{s}{2(s+1)^2 (s+2)}$$

$$= \frac{A}{s+1} + \frac{B}{(s+1)^2} + \frac{C}{s+2}$$


$$I(s) = \frac{2}{s+1} - \frac{1}{(s+1)^2} - \frac{2}{s+2}$$

$$i(t) = 2e^{-t} - t \cdot e^{-t} - 2e^{-2t}$$

Solving  
A = 2  
B = -1  
C = -2



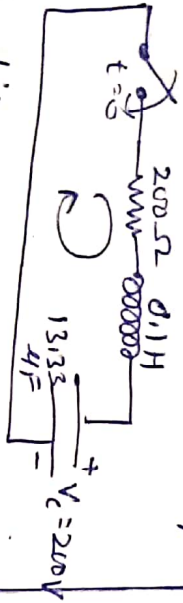For the circuit, obtain the current transient. Consider  $V_c(0^-) = 200V$ . If  $C = 10 \mu F$ , is the solution critically damped



Sol.

$$R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt = 200$$

differentiating and Rearranging

$$\frac{d^2}{dt^2} i(t) + 2000 \frac{d}{dt} i(t) + \frac{10^7}{13.33} i(t) = 0$$

Roots of this eqn. is

$$\alpha, \beta = 2000 \pm \sqrt{4000000 - \frac{4 \times 10^7}{13.33}}$$

$$= -500, -1500$$

$$\therefore i(t) = A \cdot e^{-500t} + B \cdot e^{-1500t}$$

Condition for Critically Damped  $D=0$

$$B^2 - 4ac = 4000000 - 4 \times 10^7 \frac{1}{C} = 0$$


$$\therefore C = 10 \mu F$$

$\therefore$  Yes For  $C = 10 \mu F$ , solution is Critically Damped.

Q. Find the current  $i(t)$  if the s/w is moved from a to b at time  $t=0$

Sol.

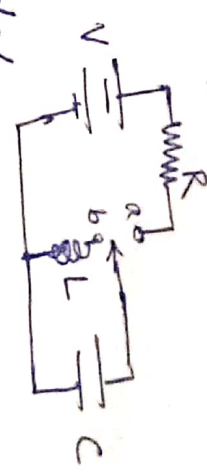When s/w is at a' for long steady state is reached and  $V_c(0^-) = V$



At time  $t=0$  s/w is moved to b' also  $i_L(0^-) = i_L(0^+) = 0$

$$\therefore L \frac{di}{dt} + \frac{1}{C} \int i dt = 0$$

Taking Laplace

$$s L I(s) - L i(0) + \frac{I(s)}{Cs} + \frac{V(0)}{s} = 0$$

Applying Initial condition

$$I(s) \left[ Ls + \frac{1}{Cs} \right] = -\frac{V}{s}$$

$$\frac{1}{s} I(s) \left[ s^2 + \frac{1}{Lc} \right] = -\frac{V}{s}$$

$$I(s) = -\frac{V}{s} \times \frac{s}{L(s^2 + \frac{1}{Lc})} = \frac{-V}{L(s^2 + \frac{1}{Lc})}$$

Taking Inverse Laplace Transform

$$I(s) = -\frac{V}{L} \times \frac{\sqrt{Lc}}{\sqrt{Lc}} \frac{1}{s^2 + (\sqrt{\frac{1}{Lc}})^2}$$

$$i(t) = -\frac{V}{L} \times \sqrt{Lc} \cdot \sin \frac{1}{\sqrt{Lc}} t$$